

# PHYSICS 1004

## Introductory Circuits Test SAMPLE



<b>Surname</b>	<b>First Name</b>
<b>SID</b>	<b>Team No. (e.g. 6ENV12)</b>
<b>The solutions to this Test can be found on the unit WebCT site under the  <i>Experimental Physics Lab and Past Examination Papers</i> links</b>	


Duration **30** minutes / Open book test / No need to show working, only the final answer is checked / All numerical answers must have appropriate units and appropriate significant figures.

### Question 1

A and B are two identical light bulbs.

If the potential difference across the battery terminals is 6 V, what is the potential difference across bulb A?

6V

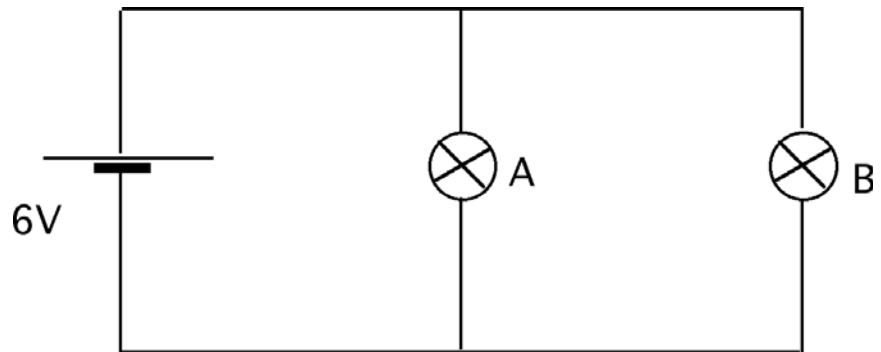

(1 mark)


### Question 2

In the circuit diagram below add meters to measure

- a) the potential difference across  $R_1$
- b) the current through  $R_2$

(1 mark)

(1 mark)

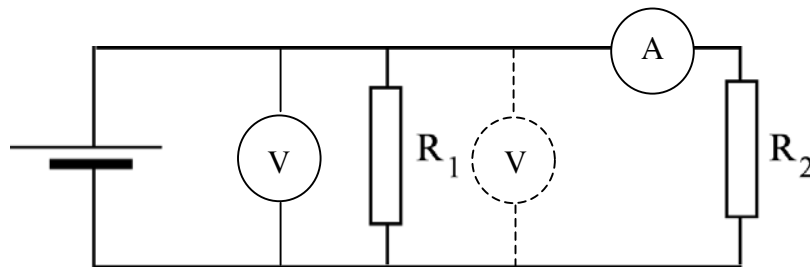


Either voltmeter position acceptable

**Question 3**

The circuit below is made up using identical light bulbs. List the light bulbs in order of increasing brightness, indicating any of equal brightness.

**D & E, A & B, C**

**(1 mark)**

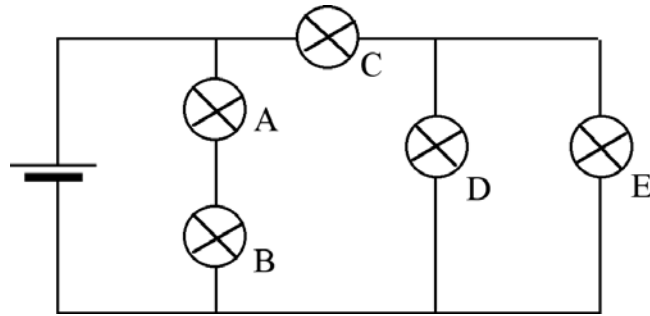

**Question 4**

A graph from an oscilloscope screen is shown below. The vertical scale is set to 0.5 V/division and the timebase to 1 ms/division. What is the period and peak-to-peak amplitude of the signal?

(a) What is the period of the signal?


**3 ms**

**(1 mark)**


(b) What is the peak-to-peak amplitude of the signal?

**2 V**

**(1 mark)**

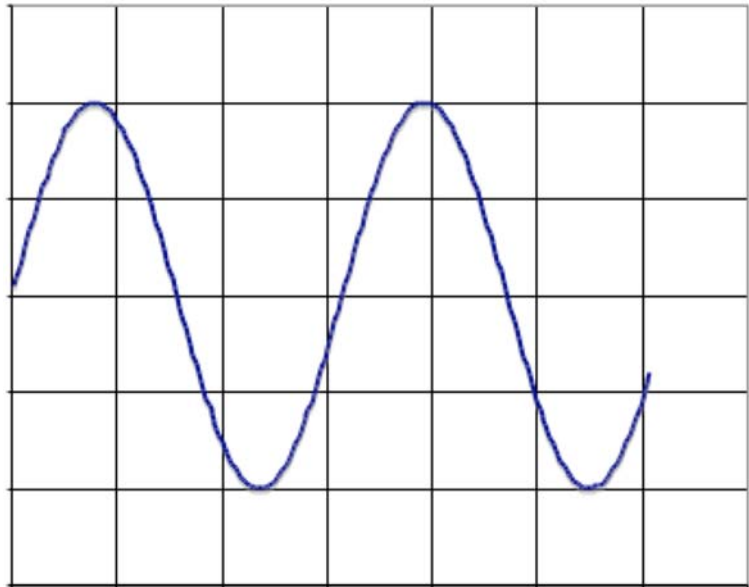

**Question 5**

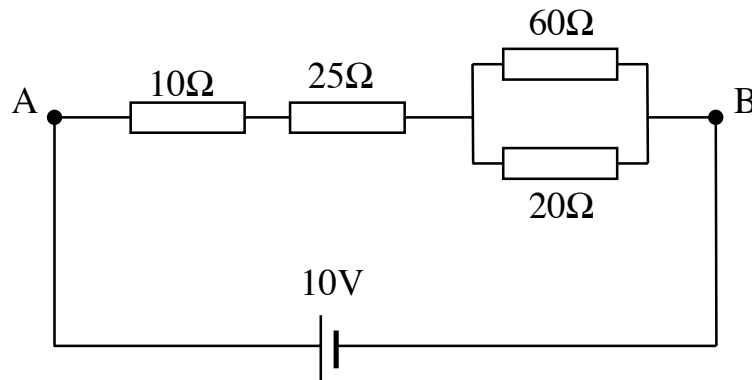

(a) What is the resistance between the terminals A and B?

**50 Ω**

**(1 mark)**

(b) Calculate the current through the 60 Ω resistor.

**0.05 A**

**(1 mark)**